

# Computer Audio Booster

Here is a simple amplifier for boosting the audio level from low-power sound cards or other audio sources driving small speakers. The circuit will deliver about 2 watts as shown.

